

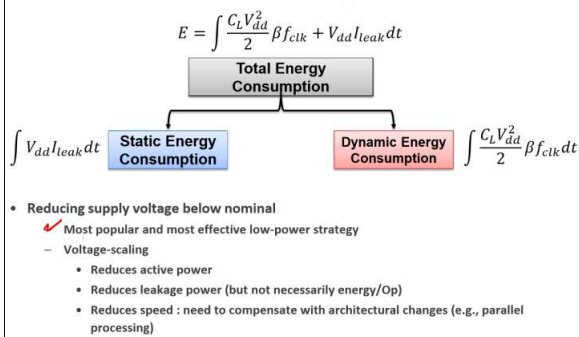


	Constant Throughput/Latency		Variable Throughput/Latency
Energy	Design Time	Non-active Modules	Run Time
Active	Logic Design Reduced V_{dd} Sizing Multi- V_{dd}	Clock Gating	DFS, DVS (Dynamic Freq, Voltage Scaling)
Leakage	+ Multi- V_T	Sleep Transistors Multi- V_{dd} Variable V_T	+ Variable V_T



Voltage Scaling

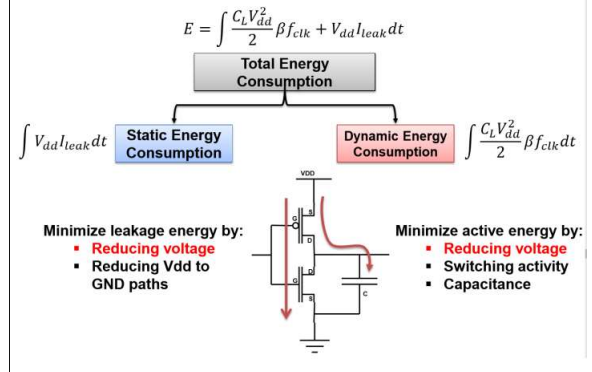

Example: StrongARM SA-1100 processor

 

CMOS Gates With Capacitive Load

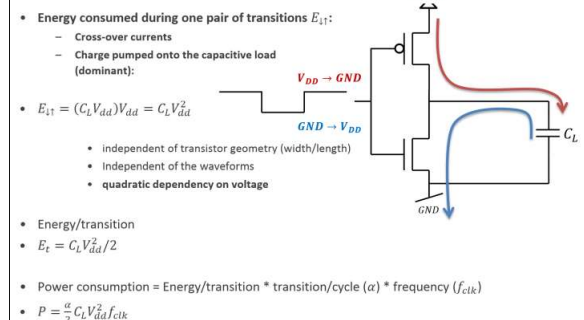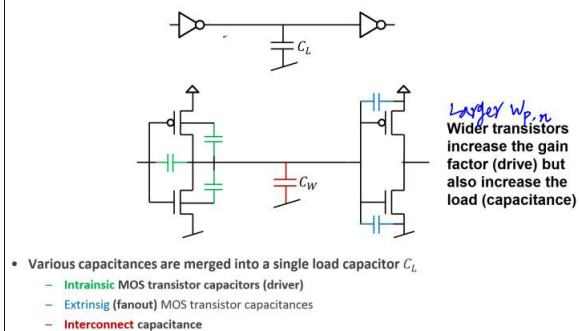

Extending our calculations to a collection of nodes

- Average energy dissipated per computation cycle for one circuit node

$$E_{ch\ k} = \frac{\alpha_k}{2} E_{ch\ cyc\ k} = \frac{\alpha_k}{2} C_k U_{dd}^2 \quad (U_{dd} = V_{dd})$$

- Average energy dissipated per computation cycle in a voltage domain of K nodes

$$E_{ch} = \sum_{k=1}^K E_{ch\ k} = U_{dd}^2 \sum_{k=1}^K \frac{\alpha_k}{2} C_k$$

Node activity (aka switching activity)

- Fact: Not all nodes within a (sub)circuit do change state at the same rate.

Definition:

A node's activity α_k indicates how many times per computation cycle node k switches from one logic state to the opposite one when averaged over many computation cycles.

Examples:

- Ungated clock in single-edge-triggered clocking: $\alpha_k = 2$
- Ungated clock in dual-edge-triggered clocking: $\alpha_k = 1$
- Output of a T-type Flip-Flop if permanently enabled: $\alpha_k = 1$
- Output of a D-type Flip-Flop fed with random data: $\alpha_k = 1/2$

Impact of Glitching

- In a synchronous (single-edge triggered) circuit, the activity factor of each node should never rise above $\alpha_k = 1/2$
- Reality: activity factors up to 6 or more can be observed:
 - Increased activity due to glitches: signals reconverge after having propagated along paths of markedly different depths
- Glitching explains why the isomorphic architecture often dissipates more (dynamic) energy than more sophisticated architectures do.
- Activity caused by glitches is very difficult to predict (depends heavily on timing)
 - Analytical prediction almost impossible

- Node activities are distributed very unevenly in most circuits.

 


Figure: Node activities in a lattice filter.

- Activity increases with the number of preceeding logic stages (increased glitching)

- Power consumption is divided into
 - Net switching power
 - Internal power
 - Internal power depends on actual input values
 - Power is consumed even if output does not change
- Library files: internal energy characterization for each cell at given supply voltage
 - Internal energy (cross-current, switching) per change in each input and output (as functions of input slope t_{tr} and output load C)
 - Contribution to capacitance of the connected net (input/output load)


$$E_{AOI}^S(B, C, D, t_{tr}) \quad E_{AOI}^R(C) \quad E_{AOI}^C(A, B, D, t_{tr}) \quad E_{AOI}^P(A, B, C, t_{tr})$$

$$C = C_{AOI}^Z + C_{net} + C_{INV}^A$$


What about the activity factor(s)?

- Fixed activity:
 - Assume a constant activity factor for all nodes in the circuit
 - Very rough estimate and highly inaccurate
- Statistical power analysis: *e.g. CREST (by F. Najm et al.)*
 - Assumes a given toggle activity at the input and propagates the activity throughout the circuit using statistical models of the gates
 - Does not account for correlation between signal values
 - No accounting for glitching activity
- Simulation based:
 - Obtains toggle statistics from gate level simulations
 - Most accurate method
 - Slow

Gate-Level Power Analysis Flow

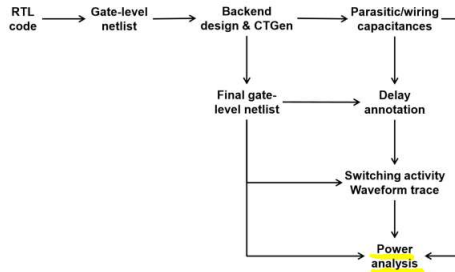

 
- The **clock** is a major source of power consumption in many synchronous designs



J. Rabaey: Power figures from sever microprocessors and DSPs

RTL Power Reduction: Clocking

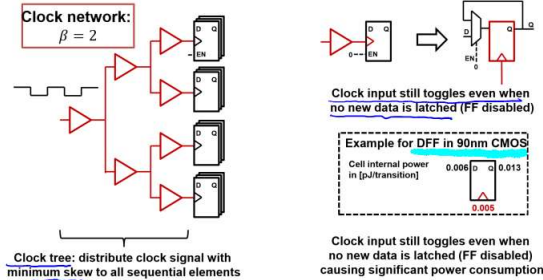
- The clock is a major source of power consumption in many synchronous designs
 - Clock distribution network (clock tree)
 - Intrinsic power of sequential elements (even when data input is constant)



RTL Power Reduction: Clocking



 
- Clock gating:** reduce power consumption by disabling the clock for
 - Inactive parts of the design (coarse grained)
 - Disabling FFs without consuming internal power (fine-grained)



RTL Power Reduction: Clocking

- Double-data rate design**
 - Clock network has the highest activity factor ($\beta = 2$)
 - Two transitions per clock period with only one transition triggering a state change

 - Replace FFs with double-edge triggered FFs (ref. C.W. Kim & S.M. Kang paper)
 - Clock frequency can be cut in $\frac{1}{2}$ for same number of operations



448

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 37, NO. 5, MAY 2002

Brief Papers

A Low-Swing Clock Double-Edge Triggered Flip-Flop

Chulwoo Kim, Member, IEEE, and Sung-Mo (Steve) Kang, Fellow, IEEE

Abstract—A low-swing clock double-edge triggered flip-flop (LSDFF) is developed to reduce power consumption significantly compared to conventional flip-flops. The LSDFF avoids unnecessary internal node transitions to reduce power consumption. In addition, power consumption in the clock tree is reduced because LSDFF uses a double-edge triggered operation as well as a low-swing clock. To prevent performance degradation of the LSDFF due to low-swing clock, low V_t transistors are used for the clocked transistors without significant leakage current problems. The power saving in flip-flop operation is estimated to be 28.6% to 49.6% with additional 78% power saving in the clock network.

To reduce power consumption in clock distribution networks, several low-swing clocking schemes have been proposed and their potential for practical applications has been shown [3], [4]. The previous half-swing scheme requires four clock signals. It suffers from skew problems among the four clock signals and requires additional chip area [4]. A reduced clock-swing flip-flop (RCSFF) requires an additional high power-supply voltage to reduce the leakage current [3]. A single-clock flip-flop for half-swing clocking does not need high power-supply voltage but has a long latency [2].

 


Fig. 3. Schematic of LSDFP.


 


Fig. 5. Simulated waveforms. (a) "0" to "1" transition of Q at rising edge of the clock. (b) "1" to "0" transition of Q at falling edge of the clock.

TABLE II
Characteristics of Full-Flips

	No. of T _h	No. of clock T _h	CK-Q (ps)	min. D-Q (ps)	Power (mW)	P-D (D)
SDFP	13	5	175	175	262	46.5
HLFP	30	4	185	180	250	47.5
CSDFP	30	5	184	180	145	34.5
LSDFP	30	5	184	180	132	26.3

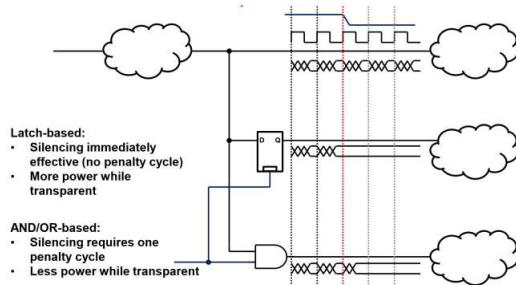- Silencing: avoid activity in unused logic
 - Unused logic is not always immediately preceded by registers
 - Avoid changes to the input of unused parts of the logic



Leakage Power

- Transistors leak currents even when in off-state


- Sources for leakage

- Sub-threshold leakage
 - Dominant component in most circuits
- Gate tunneling
 - Generally low, even in modern technologies due to high-k gate dielectrics
 - Decreases very rapidly with decreasing V_{dd}
- Junction current
 - Generally low
 - Decreases very rapidly with decreasing V_{dd}




Leakage Power

 - Long channel devices ($>130\text{nm}$): $I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}}{v_t n}}$
 - I_{DS} mostly independent from Drain-Source Voltage
 - Leakage current depends strongly on $V_{GS} - V_{th}$
 - Decreasing threshold voltage increases leakage



- Impact of technology scaling on sub-threshold leakage ($<130\text{nm}$)
 - Drain-Induced Barrier Lowering (DIBL): V_{DS} modulates threshold voltage
 - I_{DS} becomes a function of V_{DS}
 
$$I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}+\lambda_{DS}V_{DS}}{v_t n}}$$




Leakage Power over Temperature

Drain current depends exponentially on thermal voltage $v_t = kT/q$

$$I_{DS} = I_0 e^{\frac{V_{GS}-V_{th}}{v_t n}}$$

 - Exponential I_{DS} increase with temperature



Example: 0.7V, 100nm process, 15mm² die

Vivek De, Intel

Leakage in Transistor Stacks



Stacking occurs

- In many logic gates (> 1 input)
- When introduced intentionally for leakage reduction

$$I_{leak,M1} = I_0 e^{\frac{-V_M - V_{th} + \lambda_{DS} V_{dd} - V_M}{V_{th}}}$$

$$I_{leak,M2} = I_0 e^{\frac{-V_{th} + \lambda_{DS} V_M}{V_{th}}}$$

Small speed penalty: ~25%

  

Threshold Voltage Selection

- Modern process technologies support devices with different threshold voltages
 - Typically three flavors: low-VT, standard-VT, high-VT
 - Often all three flavors can be mixed in the same design

- VT-selection: tradeoff between speed and leakage

$$t_{pd} = \frac{t_{OX}}{\mu \epsilon_{OX}} \frac{L}{W} C_L \frac{V_{DD}}{(V_{DD} - V_{th})^\alpha}$$

$$I_{leak} = I_0 e^{\frac{-V_{th} + \lambda_{DS} V_{DD}}{V_{th}}}$$

- Example: 55nm process


	HVT	SVT	LVT
Delay	20ps	16ps	14ps
Leakage	30nW	60nW	200nW

Multi-VT Design

Design tradeoff when choosing a VT flavor:

- Less leakage (high-VT) increases delay and vice versa
- Threshold voltage types can often be mixed

Multi-VT design

 

- Use low-VT cells only on critical paths
- High-VT cells are used in all other paths

Caveat: can be very problematic for near-VT or sub-VT design: path delays scale very differently

Methodology:

- Either done by replacing non-critical cells in the backend OR already during synthesis by providing multiple libraries (HVT/SVT and LVT)

Body Bias Modulates Threshold Voltage

- Body of the transistor is often connected to the source (no body bias)


Introducing a body bias modulates threshold voltage

- Forward Body Bias (FBB): increases threshold voltage
- Reverse Body Bias (RBB): reduces threshold voltage

$$V_{th} = V_{th0} - \lambda_{BS} V_{BS} \quad (\eta \text{ MOS})$$

BULK CMOS:

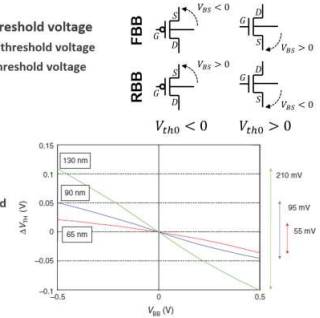
- Effect of body bias decreases for technologies below 100nm
- FBB is limited to ~300mV to avoid operating junction diodes in forward direction



Power Gating

- Avoid leakage almost completely when individual design units are not used:

 - Disconnect entire modules from the supply with headers and/or footers




Objectives with conflicting requirements

- Sleep mode: large off-resistance to avoid leakage (stacking)
 - PMOS preferred over NMOS and HVT over LVT, header/footer
- Active mode: minimize on-resistance to reduce negative impact on timing
 - Sleep transistors require large area
 - NMOS preferred over PMOS, LVT over HVT, footer-only

Power Mode Transition

- Rapid re-activation of a power gated block can cause large spikes on the supply network of the entire circuit

Popular solutions:

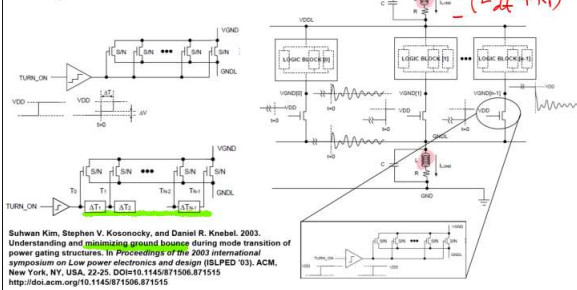

Suhwan Kim, Stephen V. Kosonocky, and Daniel R. Knebel, 2003. Understanding and minimizing ground bounce during mode transition of power gating structures. In Proceedings of the 2003 international symposium on Low power electronics and design (ISLPED '03). ACM, New York, NY, USA, 22-25. DOI:10.1145/871506.871515 <http://doi.acm.org/10.1145/871506.871515>